

实验报告

实验题目: Lab9 日期: 2018 年 11 月 23 日

姓名: 刘紫檀 学号: PB17000232 成绩: _____

实验目的:

1-1 采用门级建模方式设计 1bi 全加器, 定义门电路模型时采用参数化声明方式将基本门(与、或、非)延时设为 2 个时间单位(#2), 全加器模块调用门电路时, 传入新的延时参数: 反相器(#1)、与门(#3)、或门(#3), 编写仿真文件进行仿真——2 分

2-1 设计 8bit 增/减计数器, 通过设置综合属性, 不使用 DSP48 单元, 下载到开发板——代码 2 分, 下载 2 分

3-1 设计一精确到 0.1s 的计时器, 在七段数码管上以 M. SS. f 的格式显示, 带有复位和使能功能——代码 2 分, 下载 2 分

截图:

```
`timescale 1ns / 1ps
//1-1 全加器代码
```

```
module fulladder #(parameter INV_DELAY = 2, AND_DELAY = 2, OR_DELAY = 2) (
    input a,
    input b,
    input ci,
    output s,
    output co
);
    //s=a xor b xor ci
    wire a_xor_b;
    xor #(INV_DELAY+AND_DELAY+OR_DELAY) (a_xor_b, a, b);
    xor #(INV_DELAY+AND_DELAY+OR_DELAY) (s, a_xor_b, ci);
```

```

        //co=ab+(a xor b)ci
        wire a_b;
        wire a_xor_b_ci;
        and #(AND_DELAY) (a_b, a, b);
        and #(AND_DELAY) (a_xor_b_ci, a_xor_b, ci);
        or #(OR_DELAY) (co, a_b, a_xor_b_ci);

endmodule

```

```


`timescale 1ns / 1ps
//仿真文件

module tb();
    reg a;
    reg b;
    reg ci;
    wire s;
    wire co;

    fulladder #(1, 3, 3) DUT(a, b, ci, s, co);
    initial begin
        #50 a = 0; b = 0; ci = 0;
        #50 a = 1; b = 0; ci = 0;
        #50 a = 0; b = 1; ci = 0;
        #50 a = 0; b = 0; ci = 1;
        #50 a = 1; b = 1; ci = 0;
        #50 a = 0; b = 1; ci = 1;
        #50 a = 1; b = 0; ci = 1;
        #50 a = 1; b = 1; ci = 1;
    end
endmodule

```

实验 1-1 仿真截图

 

```

//实验 2-1 代码
`timescale 1ns / 1ps
(* use_dsp48 = "no" *)
module bcd_decoder(
    input [3:0] x,
    output reg [6:0] seg,

```

```

        output reg [6:0] seg_hi
    );

always @ (*)
begin
    case (x)
        4'd0: begin seg = 7'b1000000; seg_hi = 7'b1000000; end
        4'd1: begin seg = 7'b1111001; seg_hi = 7'b1000000; end
        4'd2: begin seg = 7'b0100100; seg_hi = 7'b1000000; end
        4'd3: begin seg = 7'b0110000; seg_hi = 7'b1000000; end
        4'd4: begin seg = 7'b0011001; seg_hi = 7'b1000000; end
        4'd5: begin seg = 7'b0010010; seg_hi = 7'b1000000; end
        4'd6: begin seg = 7'b0000010; seg_hi = 7'b1000000; end
        4'd7: begin seg = 7'b1111000; seg_hi = 7'b1000000; end
        4'd8: begin seg = 7'b0000000; seg_hi = 7'b1000000; end
        4'd9: begin seg = 7'b0010000; seg_hi = 7'b1000000; end
        4'd10: begin seg = 7'b1000000; seg_hi = 7'b1111001; end
        4'd11: begin seg = 7'b1111001; seg_hi = 7'b1111001; end
        4'd12: begin seg = 7'b0100100; seg_hi = 7'b1111001; end
        4'd13: begin seg = 7'b0110000; seg_hi = 7'b1111001; end
        4'd14: begin seg = 7'b0011001; seg_hi = 7'b1111001; end
        4'd15: begin seg = 7'b0010010; seg_hi = 7'b1111001; end
    endcase

end

endmodule

```

```

(* use_dsp48 = "no" *)
module main(
    input clk_in1,
    input reset,
    input enable,
    input dec,
    output locked,
    output [7:0] led
);
    wire sig; //flush signal
    wire sig_inc;
    wire counter_carry;

    wire clkabc; //divided signal
    clk_wiz_0 clk_module (
        .clk_out1(clkabc),

```

```

        .reset(0),
        .locked(locked),
        .clk_in1(clk_in1));
sec_gen s_gen(.clk_out1(clkabc), .sig(sig_inc), .enable(enable), .reset(0));
c_counter_binary_0 counter (
    .CLK(sig_inc),          // input wire CLK
    .CE(enable),            // input wire
    .SCLR(reset),
    .UP(dec),
    .Q(led)                 // output wire [3 : 0] Q
);

endmodule

(* use_dsp48 = "no" *)
module sec_gen(
    input clk_out1,
    input enable,
    output reg sig,
    input reset
);
reg [31:0] count; //Can't be in procedural statements

always @ (posedge clk_out1 or posedge reset)
begin
    if (reset) begin
        sig <= 1'b0;
        count <= 32'd2500000;
    end
    else if (enable) begin
        //NOTE: if (enable) begin WILL CAUSE BUG on reset=enable=1, causing count
        undefined
        if (count == 0) begin
            sig <= ~sig;
            count <= 32'd2500000;
        end else count <= count - 1;
    end
end
endmodule

module c_counter_binary_0 #(parameter COUNT_SIZE = 233) (input CLK, input CE, input
SCLR, input UP, output reg [7:0] Q);
    always @ (posedge CLK) begin
        if (SCLR)

```

```

        Q <= 8'b00000000;
    else begin
        if (CE) begin
            if (Q >= COUNT_SIZE)
                Q <= 8'b00000000;
            else if (Q == 0 && DOWN)
                Q <= COUNT_SIZE;
            else begin
                if (UP) begin
                    Q <= Q + 1;
                end else begin
                    Q <= Q - 1;
                end
            end
        end
    end
end
endmodule

```

实验 2-1 下载照片



实验 2-1 Summary

Resource	Utilization	Available	Utilization...
LUT	80	63400	0.13
FF	41	126800	0.03
IO	13	210	6.19
BUFG	2	32	6.25
MMCM	1	6	16.67

Number of BUFG/BUFGCTRL: 2

Number of Slice LUTs used: 80

Number of FF used: 41

Number of DSP48E1 slices used: 0

Number of IOs used: 13

实验 3-1

//代码

```
`timescale 1ns / 1ps
```

```
module bcd_decoder(
```

```
    input [3:0] x,
```

```
    output reg [6:0] seg,
```

```
    output reg [6:0] seg_hi
```

```
);
```

```
always @ (*)
```

```
begin
```

```
    case (x)
```

```
        4'd0: begin seg = 7'b1000000; seg_hi = 7'b1000000; end
```

```
        4'd1: begin seg = 7'b1111001; seg_hi = 7'b1000000; end
```

```
        4'd2: begin seg = 7'b0100100; seg_hi = 7'b1000000; end
```

```
        4'd3: begin seg = 7'b0110000; seg_hi = 7'b1000000; end
```

```
        4'd4: begin seg = 7'b0011001; seg_hi = 7'b1000000; end
```

```
        4'd5: begin seg = 7'b0010010; seg_hi = 7'b1000000; end
```

```
        4'd6: begin seg = 7'b0000010; seg_hi = 7'b1000000; end
```

```
        4'd7: begin seg = 7'b1111000; seg_hi = 7'b1000000; end
```

```
        4'd8: begin seg = 7'b0000000; seg_hi = 7'b1000000; end
```

```
        4'd9: begin seg = 7'b0010000; seg_hi = 7'b1000000; end
```

```
        4'd10: begin seg = 7'b1000000; seg_hi = 7'b1111001; end
```

```
        4'd11: begin seg = 7'b1111001; seg_hi = 7'b1111001; end
```

```
        4'd12: begin seg = 7'b0100100; seg_hi = 7'b1111001; end
```

```
        4'd13: begin seg = 7'b0110000; seg_hi = 7'b1111001; end
```

```
        4'd14: begin seg = 7'b0011001; seg_hi = 7'b1111001; end
```

```
        4'd15: begin seg = 7'b0010010; seg_hi = 7'b1111001; end
```

```

        endcase

end

endmodule


module carry_ff(input clk_div, input counter_carry, output reg carry_pulse);
    //Negedge of counter_carry detector
    //Skew and delay: 1 cycle (1/5000000 sec.)
    reg cc_prev;
    always @ (posedge clk_div) begin
        if (carry_pulse == 0 && cc_prev == 1)
            carry_pulse <= 1;
            cc_prev <= counter_carry;
        if (cc_prev == counter_carry)
            carry_pulse <= 0;
    end
endmodule


module main(
    input clk_in1,
    input reset,
    input enable,
    output locked,
    output reg [6:0] seg,
    output reg [7:0] an,
    output reg digit_dot
);
    wire [1:0] sig; //flush signal
    wire sig_inc; //increment signal
    wire clk_div; //5MHz Clock signal


    wire [3:0] low_bcd;
    wire [3:0] hi_bcd;
    wire [3:0] six_bcd;
    wire [3:0] five_bcd;


    wire [6:0] seg_temp_low;
    wire [6:0] seg_temp_hi;
    wire [6:0] seg_temp_six;
    wire [6:0] seg_temp_five;

```

```

bcd_decoder low_decode(low_bcd, seg_temp_low);
bcd_decoder hi_decode(hi_bcd, seg_temp_hi);
bcd_decoder six_decode(six_bcd, seg_temp_six);
bcd_decoder five_decode(five_bcd, seg_temp_five);

//flush signal generator
flush_gen f_gen(.clk_div(clk_div), .sig(sig), .reset(0));

clk_wiz_0 c_clk(
    .clk_out1(clk_div),      // output clk_out1
    .reset(0), // input reset
    .locked(locked),        // output locked
    .clk_in1(clk_in1));     // input clk_in1

c_counter_pulsegen sig_gen (
    .CLK(clk_div),          // input wire CLK
    .CE(enable),            // input wire CE
    .THRESH0(sig_inc) // output wire THRESH0
);

wire counter_carry;

// .1s counter ( 0 ~ 9 )
c_counter_dec low_counter (
    .CLK(clk_div),          // input wire CLK
    .CE(sig_inc),           // input wire CE
    .SCLR(reset),           // input wire SCLR
    .THRESH0(counter_carry), // output wire THRESH0
    .Q(low_bcd)             // output wire [3 : 0] Q
);

wire carry_pulse_1;
carry_ff c_ff_1
(.clk_div(clk_div), .counter_carry(counter_carry), .carry_pulse(carry_pulse_1));

wire counter_carry_1;
// 1s counter ( 0 ~ 9 )
c_counter_dec hi_counter (
    .CLK(clk_div),          // input wire CLK
    .SCLR(reset),           // input wire SCLR
    .CE(carry_pulse_1),     // input wire CE
    .THRESH0(counter_carry_1), // output wire THRESH0
    .Q(hi_bcd)             // output wire [3 : 0] Q
);

```



```

    wire carry_pulse_2;
    carry_ff c_ff_2
(.clk_div(clk_div), .counter_carry(counter_carry_1), .carry_pulse(carry_pulse_2
));

```

```

    wire counter_carry_2;
    // 10s counter ( 0 ~ 9 )
    c_counter_six six_counter (
        .CLK(clk_div),          // input wire CLK
        .SCLR(reset),          // input wire SCLR
        .CE(carry_pulse_2),      // input wire CE
        .THRESH0(counter_carry_2), // output wire THRESH0
        .Q(six_bcd)             // output wire [3 : 0] Q
    );

```

```

    wire carry_pulse_3;
    carry_ff c_ff_3
(.clk_div(clk_div), .counter_carry(counter_carry_2), .carry_pulse(carry_pulse_3
));

```

```

    wire counter_carry_3;
    // Min counter ( 0 ~ 4 )
    c_counter_five five_counter (
        .CLK(clk_div),          // input wire CLK
        .SCLR(reset),          // input wire SCLR
        .CE(carry_pulse_3),      // input wire CE
        .THRESH0(counter_carry_3), // output wire THRESH0
        .Q(five_bcd)             // output wire [3 : 0] Q
    );

```

```

    always @ (clk_div) begin
        case (sig)
            2'b00: begin seg <= seg_temp_low;  an <= 8'b11111110; digit_dot <= 1;
end
            2'b01: begin seg <= seg_temp_hi;  an <= 8'b11111101; digit_dot <= 0; end
            2'b10: begin seg <= seg_temp_six;  an <= 8'b11111011; digit_dot <= 1;
end
            2'b11: begin seg <= seg_temp_five; an <= 8'b11110111; digit_dot <= 0;
end
        endcase
    end

```

```
endmodule

module flush_gen (input clk_div, input reset, output reg [1:0] sig);
    reg [31:0] count;
    always @ (posedge clk_div) begin
        if (reset)
            count <= 0;
        else if (count == 32'd5000) begin
            count <= 0;
            sig <= sig + 1;
        end else count <= count + 1;
    end
endmodule
```

实验 3-1 下载截图

（在刷新，快门没那么快，所以最后一位重影了）



实验总结：本次实验我熟练掌握了 IP Counter 的构建。