

实验报告

实验题目: Lab10 日期: 2018 年 11 月 30 日

姓名: 刘紫檀 学号: PB17000232 成绩: _____

实验目的:

- 1-1 使用三段式 Mealy 型 FSM 实现一个序列检测器, 当接收到的 1 的总数为 3 的整数倍时, 输出为 1, 否则输出 0。编写代码 2 分、仿真 2 分、下载 2 分。
- 2-1 使用三段式 Moore 型 FSM 实现一个序列检测器, 序列为 01/00 时输出为 0, 序列为 11/00 时输出为 1, 序列为 10/00 时输出反转, 否则输出保持不变。编码 2 分、仿真 2 分、下载 2 分

截图:

```
//实验 1-1 代码
`timescale 1ns / 1ps

// 0 -> 1 -> 2
//(1) (0) (0)
//a=1 represents the [next] state prediction..
//receiving 0 will cause the circ hang at their current state

module seq_detect(
    input ain,
    input clk,
    input rst,
    output reg yout,
    output reg [3:0] count
);
    reg [1:0] state;
    reg [1:0] next_state;
    reg count_carry;
    always @ (posedge clk or negedge rst) begin
        if (rst) begin
```

```

        state <= 2'b00;
        count <= 4'b0000;
    end else begin
        state <= next_state;
        count <= count + count_carry;
    end
end

always @ (state or ain) begin //next_state
    count_carry = 0;
    case(state)
        2'b00: if (ain == 1) begin next_state = 2'b01; count_carry = 1; end else
next_state = 2'b00;
        2'b01: if (ain == 1) begin next_state = 2'b10; count_carry = 1; end else
next_state = 2'b01;
        2'b10: if (ain == 1) begin next_state = 2'b00; count_carry = 1; end else
next_state = 2'b10;
        //illegal
        2'b11: next_state = 2'b00;
    endcase
end

always @ (state or ain) begin //output
    case(state)
        2'b00: if (ain == 1) yout = 0; else yout = 1;
        2'b01: yout = 0;
        2'b10: if (ain == 1) yout = 1; else yout = 0;
        default: yout = 1; //SHOULD NEVER REACH THIS
    endcase
end

endmodule

//实验 1-1 Testbench
`timescale 1ns / 1ps

module seq_detect_tb();

    reg ain;
    reg clk;
    reg rst;
    wire [3:0] count;
    wire yout;
    seq_detect DUT(ain, clk, rst, yout, count);


```

```
initial begin clk = 0; end
always #5 clk=~clk;
initial begin
    ain = 0;
    rst = 1;
    #20 rst = 0;
    #20 ain = 1;
    #20 ain = 0;
    #60 ain = 1;
    #40 ain = 0;
    #20 ain = 1;


end
```

```
endmodule
```

实验 1-1 仿真截图

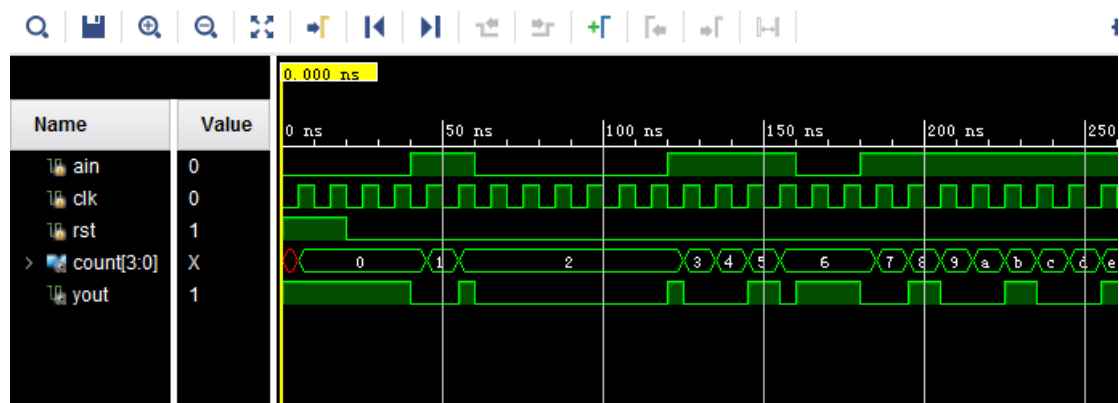

实验 1-1 下载截图

 

```

//实验 2-1 代码
`timescale 1ns / 1ps
/* States variable is designed as {out, prev[1], prev[0]} */

module seq_detect_moore(
    input [1:0] ain,
    input clk,
    input rst,
    output reg yout);

    reg out;
    reg [1:0] prev;
    reg next_out;
    reg [1:0] next_prev;
    always @ (posedge clk or negedge rst) begin
        if (rst) begin
            out <= 0;
            prev <= 2'b00;
        end else begin
            out <= next_out;
            prev <= next_prev;
        end
    end

    always @ (out) begin
        yout = out;
    end

    always @ (out, prev, ain) begin
        case ({out, prev[1], prev[0]})
            3'b000:
                next_out = out;
            3'b100:
                next_out = out;
            3'b001:
                case (ain)
                    2'b00: next_out = 0;
                    default: next_out = out;
                endcase
            3'b101:
                case (ain)
                    2'b00: next_out = 0;
                    default: next_out = out;
                endcase
        endcase
    end

```

```

        3'b010:
            case (ain)
                2'b00: next_out = 1;
                default: next_out = out;
            endcase
        3'b110:
            case (ain)
                2'b00: next_out = 0;
                default: next_out = out;
            endcase
        3'b011:
            case (ain)
                2'b00: next_out = 1;
                default: next_out = out;
            endcase
        3'b111:
            case (ain)
                2'b00: next_out = 1;
                default: next_out = out;
            endcase
    endcase
    next_prev = ain;
end

endmodule

//实验 2-1 Testbench
`timescale 1ns / 1ps

module seq_detect_tb();

    reg [1:0] ain;
    reg clk;
    reg rst;
    wire yout;
    seq_detect_moore DUT(ain, clk, rst, yout);
    initial begin clk = 0; end
    always #5 clk=~clk;
    initial begin
        ain = 2'b00;
        rst = 1;
        #20 rst = 0;
        #20 ain = 2'b11;
        #10 ain = 2'b10;
    end

```


```

#10 ain = 2'b00;
#20 ain = 2'b10;
#10 ain = 2'b00;
#10 ain = 2'b11;
#10 ain = 2'b00;
#10 ain = 2'b01;
#10 ain = 2'b00;
#10 ain = 2'b10;
#10 ain = 2'b11;
#10 ain = 2'b00;
#30 ain = 2'b10;

```

end

endmodule

 

实验 2-1 仿真截图



实验 2-1 下载截图

实验总结：这次实验我了解了状态机在 Verilog 中的实现方法。